

运算器及其应用


李卓 pb19000064

实验目的

- 掌握算术逻辑单元 (ALU) 的功能
- 掌握数据通路和控制器的设计方法
- 掌握组合电路和时序电路，以及参数化和结构化的 Verilog 描述方法
- 了解查看电路性能和资源使用情况


实验原理

一， ALU

 


a b 为两个 32/6 位操作数，F 为操作功能数，y 为 32/6 结果, z 为 0 标志

二， FLS

 

en 为输入输出使能信号，rst 复位，d 输入数列初始项，f 输出数列

三, ALU 分时复用

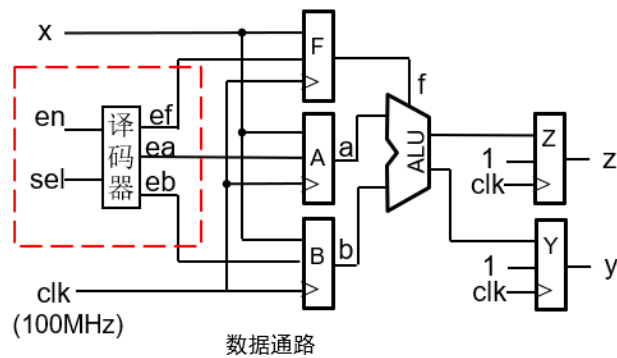


操作数 a, b 和功能 f 复用开关输入 x[5:0]。方法：通过 sel 和 en，生成译码电路，将开关输入 x[5:0]分时存入寄存器 F(x[2:0]), A(x[5:0]), B(x[5:0])


实验思路

—, ALU

文件结构如下

 

数据通路如下:

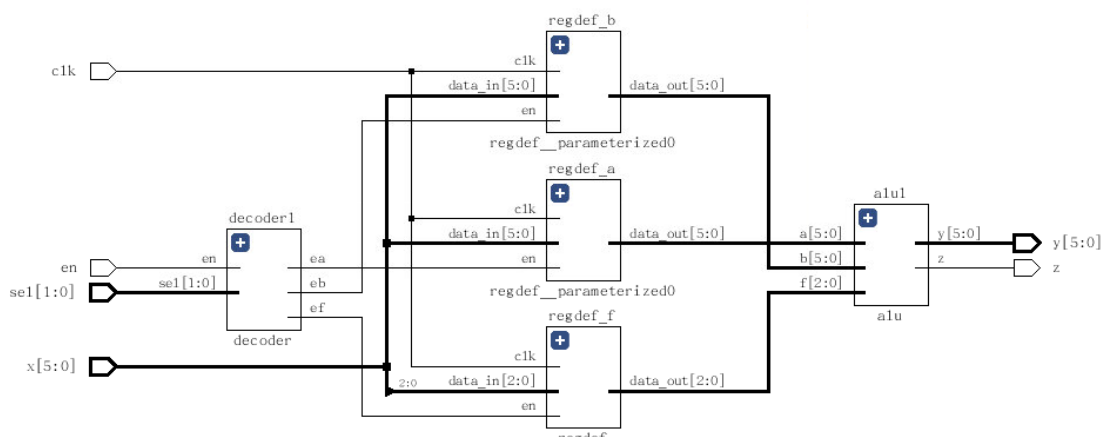

二, FLS

一个寄存器 S 存储当前状态

状态转移图: $s_0 \rightarrow s_1 \rightarrow s_2 \rightarrow s_3 \leftarrow s_4$

s_0 为初始态, 复位后为 s_0 , $s_1 s_2$ 接受输入的 d 值,

$s_3 s_4$ 计算 $F(n) F(n-1) F(n-2)$ 的值

$F(n-1) F(n-2)$ 存储在寄存器 a b 中 输出 $f=a+b$

中间寄存器 tmp0 tmp1 存储 a b 相关的转移值

实验代码

1.

```
module alu#(
    parameter WIDTH = 6
)(
    input[WIDTH-1:0] a,b,
    input[2:0] f,
    output reg [WIDTH-1:0] y,
    output reg z
);

always@(*)
begin
    case(f)
```

```

        3'b000: y=a+b;

        3'b001: y=a-b;

        3'b010: y=a&b;

        3'b011: y=a|b;

        3'b100: y=a^b;

        default: y=0;

    endcase

    if(!y)

        z=1;

    else

        z=0;

    end

endmodule

```

2.

```

module alu_test#(

parameter WIDTH = 6

)(

input en,    //button

input clk,  //

```

```
input [1:0] sel,    //sw7~6

input [WIDTH - 1:0] x,  //sw5~0

output z,

output [WIDTH - 1:0] y

    );
```

```
wire ef;
```

```
wire ea,eb;
```

```
wire [2:0] a_f;
```

```
wire [WIDTH-1:0] a_a,a_b;
```

```
reg [31:0] num;
```

```
reg [2:0] cnt;
```

```
reg [3:0]hexplay_an;
```

```
reg [3:0]hexplay_data;
```

```
always @(posedge clk)
```

```
begin
```

```
    if(num[20]==1)
```

```
    begin
```

```
        cnt<=cnt+1;
```

```
        num<=0;
```

```

        end

        else

            num<=num+1;

        end

    always @(*)

    begin

        case(cnt)

            3'b000: begin hexplay_an<=0;hexplay_data<=5;end

            3'b001: begin hexplay_an<=1;hexplay_data<=9;end

            3'b010: begin hexplay_an<=2;hexplay_data<=0;end

            3'b011: begin hexplay_an<=3;hexplay_data<=3;end

            3'b100: begin hexplay_an<=4;hexplay_data<=1;end

            3'b101: begin hexplay_an<=5;hexplay_data<=8;end

            3'b110: begin hexplay_an<=6;hexplay_data<=2;end

            3'b111: begin hexplay_an<=7;hexplay_data<=6;end

        endcase

    end

```

```

decoder #(.WIDTH(2))decoder1(.en(en),.sel(sel),.ef(ef),.ea(ea),.eb(eb));

```

```

alu #(.WIDTH(6))alu1(.a(a_a),.b(a_b),.f(a_f),.y(y),.z(z));

```

```

regdef #(.WIDTH(3))regdef_f(.clk(clk),.en(ef),.data_in(x[2:0]),.data_out(a_f));

regdef #(.WIDTH(6))regdef_a(.clk(clk),.en(ea),.data_in(x),.data_out(a_a));

regdef #(.WIDTH(6))regdef_b(.clk(clk),.en(eb),.data_in(x),.data_out(a_b));


endmodule

```

3.

```

module decoder#(
parameter WIDTH = 2
)(
input en,
input [WIDTH-1:0] sel,
output reg ef,
output reg ea,
output reg eb
);

always@(*)

begin

```

```

if(!en)

begin

    ef = 0; ea = 0; eb = 0;

end

else

    case(sel)

        2'b10: begin ef=1; ea=0; eb=0; end

        2'b00: begin ef=0; ea=1; eb=0; end

        2'b01: begin ef=0; ea=0; eb=1; end

        default: begin ef=0; ea=0; eb=0; end

    endcase

end

endmodule

```

4.

```

module fls#(

parameter WIDTH = 7

)(

    input clk,

```



```
    input rst,  
  
    input en,  
  
    input [WIDTH-1:0] d,  
  
    output [WIDTH-1:0] f  
);
```

```
reg [WIDTH-1:0] a,b;  
  
reg [WIDTH-1:0] tmp1,tmp2;  
  
reg flag=0;  
  
reg [2:0] curr_state;  
  
reg [2:0] next_state;
```

```
parameter [2:0] ALU_ADD = 3'b000;  
  
parameter S0=3'b000;  
  
parameter S1=3'b001;  
  
parameter S2=3'b010;  
  
parameter S3=3'b011;  
  
parameter S4=3'b100;
```

```
reg en_r1,en_r2;  
  
wire en_edge;  
  
always@(posedge clk)
```

```

        en_r1<=en;

always@(posedge clk)

    en_r2<=en_r1;

assign en_edge = en_r1&(~en_r2);


alu #(.WIDTH(7))alu1(.a(a),.b(b),.f(ALU_ADD),.y(f),.z());


always@(*)

begin

    case(curr_state)

        S0: next_state=S1;

        S1: next_state=S2;

        S2: next_state=S3;

        S3: next_state=S4;

        S4: next_state=S3;

        default: next_state=S0;

    endcase

end


always@(posedge clk)

begin

    if(!en_edge)

```

```

        flag<=0;

    else

        flag<=1;

    end

always@(posedge clk)

begin

    if(rst)

        curr_state <= S0;

    else if(!flag)

        if(en_edge)

            curr_state <=next_state;

    end

always@(posedge clk)

begin

    if(en_edge&(!flag))

    begin

        case(curr_state)

        S0:begin a=0;b=0;tmp1=0;tmp2=0;end

        S1:begin a=d;b=0;tmp1=a;end

        S2:begin a=0;b=d;tmp2=b;end

        S3:begin a=tmp1;b=tmp2;tmp1=a+b;end

```

```
S4:begin a=tmp1;b=tmp2;tmp2=a+b;end
```

```
endcase
```

```
end
```

```
end
```

```
endmodule
```